

**RAMCO INSTITUTE OF TECHNOLOGY**  
**Department of Electronics and Communication Engineering**  
**Academic Year: 2017 - 2018 (Odd Semester)**

**Innovative Practices Description**

**Degree, Semester & Branch:** VII Semester B.E. ECE A  
**Course Code & Title:** EC6701 RF and Microwave Engineering  
**Name of the Faculty member:** Mrs.V.SrIREngaNachiyar  
**Name of the Topic:** Z,Y,h & ABCD parameter  
**Name of the Innovative Practice:** Online quiz

**Description:**

A two-port network (a kind of four-terminal network or quadripole) is an **electrical network** (circuit) or device with two pairs of terminals to connect to external circuits. Two terminals constitute a **port** if the currents applied to them satisfy the essential requirement known as the port condition: the **electric current** entering one terminal must equal the current emerging from the other terminal on the same port.

**Impedance parameters (z-parameters)**

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

where

$$\begin{aligned} z_{11} &\stackrel{\text{def}}{=} \left. \frac{V_1}{I_1} \right|_{I_2=0} & z_{12} &\stackrel{\text{def}}{=} \left. \frac{V_1}{I_2} \right|_{I_1=0} \\ z_{21} &\stackrel{\text{def}}{=} \left. \frac{V_2}{I_1} \right|_{I_2=0} & z_{22} &\stackrel{\text{def}}{=} \left. \frac{V_2}{I_2} \right|_{I_1=0} \end{aligned}$$

**Admittance parameters (y-parameters)**

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where

$$\begin{aligned} y_{11} &\stackrel{\text{def}}{=} \left. \frac{I_1}{V_1} \right|_{V_2=0} & y_{12} &\stackrel{\text{def}}{=} \left. \frac{I_1}{V_2} \right|_{V_1=0} \\ y_{21} &\stackrel{\text{def}}{=} \left. \frac{I_2}{V_1} \right|_{V_2=0} & y_{22} &\stackrel{\text{def}}{=} \left. \frac{I_2}{V_2} \right|_{V_1=0} \end{aligned}$$

**Hybrid parameters (h-parameters)**

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

where

$$\begin{aligned} h_{11} &\stackrel{\text{def}}{=} \left. \frac{V_1}{I_1} \right|_{V_2=0} & h_{12} &\stackrel{\text{def}}{=} \left. \frac{V_1}{V_2} \right|_{I_1=0} \\ h_{21} &\stackrel{\text{def}}{=} \left. \frac{I_2}{I_1} \right|_{V_2=0} & h_{22} &\stackrel{\text{def}}{=} \left. \frac{I_2}{V_2} \right|_{I_1=0} \end{aligned}$$

**ABCD-parameters**

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

where

$$\begin{aligned} A &\stackrel{\text{def}}{=} \left. \frac{V_1}{V_2} \right|_{I_2=0} & B &\stackrel{\text{def}}{=} \left. -\frac{V_1}{I_2} \right|_{V_2=0} \\ C &\stackrel{\text{def}}{=} \left. \frac{I_1}{V_2} \right|_{I_2=0} & D &\stackrel{\text{def}}{=} \left. -\frac{I_1}{I_2} \right|_{V_2=0} \end{aligned}$$

**References:**

1. [https://en.wikipedia.org/wiki/Two-port\\_network#Impedance\\_parameters\\_\(z-parameters\)](https://en.wikipedia.org/wiki/Two-port_network#Impedance_parameters_(z-parameters))
2. Annapurna Das and Sisir K Das, "Microwave Engineering"
3. Reinhold Ludwig and Gene Bogdanov, "RF Circuit Design: Theory and Applications"